

RECTIFIERS

Rectification :-

Rectification is the process of converting alternating current (ac) into direct current(dc).

Rectifier :-

Rectifier is a device that converts ac (alternating current) into dc (direct current). Semiconductor diodes are used as rectifying elements.

Rectifiers are classified into :



- 1. Half wave rectifier (HWR)**
- 2. Full wave rectifier (FWR)**

Full wave rectifier can be built in two ways :

1. Full – wave rectifier using two diodes and a centre tapped transformer
2. Full-wave bridge rectifier using four diodes and an ordinary transformer.

(FWBR)

HALFWAVE RECTIFIER (HWR):-

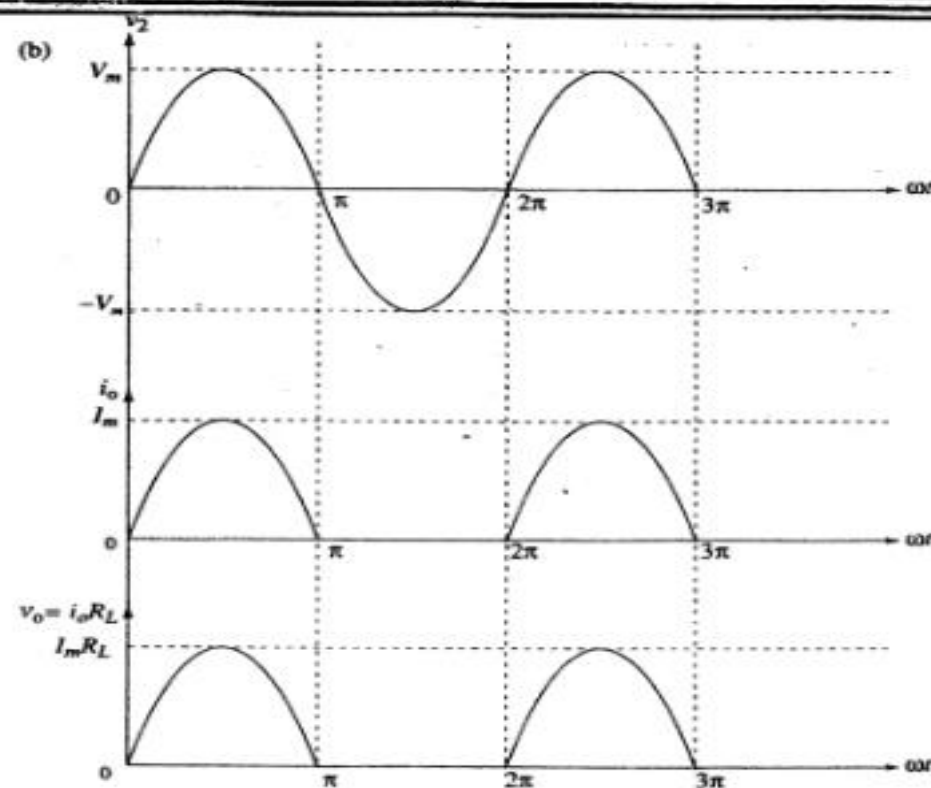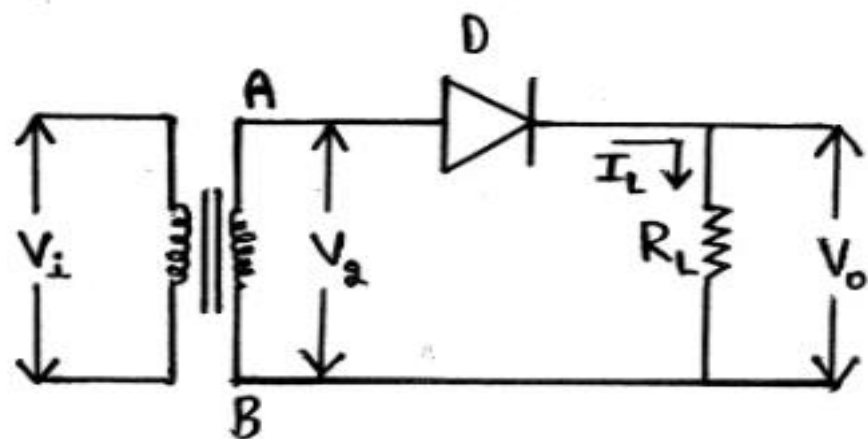

(a) Half-wave rectifier. (b) Waveforms of transformer secondary voltage, load current and load voltage.

Half wave rectifier consists of a single diode in series with load resistance. The ac voltage across the secondary winding A & B changes polarities after half cycle.

Operation :-

During positive half cycle of the ac input voltage, end A becomes positive with respect to end B, the diode 'D' is forward biased and acts as a short circuit, thus the current flows in the circuit, Figure 2. The load voltage is given by $V_0 = I_L R_L$.

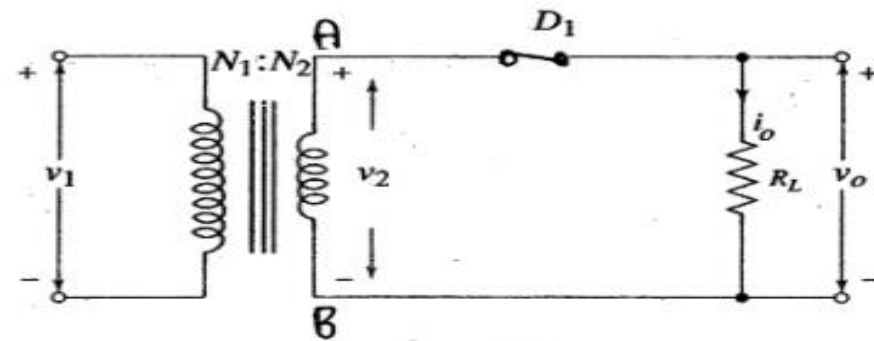


Fig ②

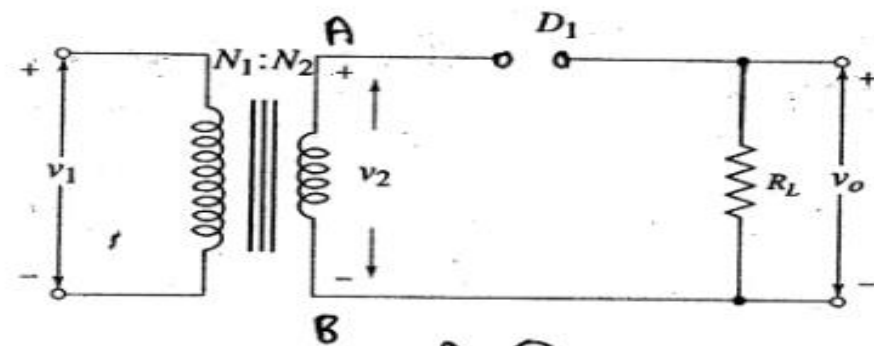


Fig ③

During negative half cycle of the ac input voltage, end A becomes

During negative half cycle of the ac input voltage, end A becomes negative with respect to end B, the diode 'D' is reverse biased and acts as an open circuit, thus **NO current** flows in the circuit, Figure 3. The load voltage is given by $V_0 = 0 \times R_L$.

Therefore

$$V_0 = 0 \text{ v}$$

The dc output waveform is **expected** to be a **straight line** but the half wave rectifier gives output in the form of positive sinusoidal pulse. Hence the output is called **pulsating dc**.

The load current is given by :

$$I_L = \begin{cases} I_m \sin \omega t & 0 \leq \omega t \leq \pi \\ 0 & \pi \leq \omega t \leq 2\pi \end{cases}$$

Where

$$I_m = \frac{V_m}{R_L}$$

1) Average or dc load current (I_{dc} or I_{av}) :-

$$\begin{aligned} I_{dc} &= \frac{1}{2\pi} \int_0^{2\pi} I_L \, d\omega t \\ &= \frac{1}{2\pi} \int_0^{2\pi} I_m \sin \omega t \, d\omega t \\ &= \frac{1}{2\pi} \left[\int_0^{\pi} I_m \sin \omega t \, d\omega t + \int_{\pi}^{2\pi} 0 \, d\omega t \right] \\ &= \frac{I_m}{2\pi} \int_0^{\pi} \sin \omega t \, d\omega t \\ &= \frac{I_m}{2\pi} \left[-\cos \omega t \right]_0^{\pi} \\ &= -\frac{I_m}{2\pi} \left[\cos(\pi) - \cos(0) \right] \\ &= -\frac{I_m}{2\pi} \left[-1 - 1 \right] \\ &= -\frac{I_m}{2\pi} (-2) \\ &= \frac{2I_m}{2\pi} \end{aligned}$$

$$\boxed{I_{dc} = \frac{I_m}{\pi}}$$

2) Average dc load voltage (V_{dc}) :-

$$\begin{aligned} V_{dc} &= I_{dc} R_L \\ &= \frac{I_m}{\pi} R_L \\ &= \frac{V_m}{\cancel{R_L} \cdot \pi} \cancel{R_L} \end{aligned}$$

$$\boxed{V_{dc} = \frac{V_m}{\pi}}$$

$$\boxed{I_{dc} = \frac{I_m}{\pi}}$$

$$\boxed{I_m = \frac{V_m}{R_L}}$$

3) RMS value of load current (I_{RMS}) :-

$$I_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_L^2 d\omega t}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (I_m \sin \omega t)^2 d\omega t}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2 \omega t \cdot d\omega t}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} \frac{1 - \cos 2\omega t}{2} \cdot d\omega t}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left[\int_0^{\pi} 1 - \cos 2\omega t \cdot d\omega t + \int_{\pi}^{2\pi} 1 - \cancel{\cos}^0 2\omega t \cdot d\omega t \right]}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left[\theta - \frac{\sin 2\omega t}{2} \right]_0^{\pi}}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left\{ [\theta]_0^{\pi} - \left[\frac{\sin 2\omega t}{2} \right]_0^{\pi} \right\}}$$

$$\boxed{\begin{aligned} \sin^2 \theta &= \frac{1 - \cos 2\theta}{2} \\ \int \cos 2\theta &= \frac{\sin 2\theta}{2} \end{aligned}}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left\{ \left[0 \right]_0^\pi - \left[\frac{\sin 2\omega t}{2} \right]_0^\pi \right\}}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left\{ [\pi - 0] - \left[\frac{\sin 2(\pi)}{2} - \frac{\sin 2(0)}{2} \right] \right\}}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \cdot \pi} = \sqrt{\frac{I_m^2}{4}}$$

$$\boxed{I_{RMS} = \frac{I_m}{2}}$$

4) RMS value of the load voltage (V_{RMS}) :-

$$\begin{aligned} V_{RMS} &= I_{RMS} R_L \\ &= \frac{I_m}{2} R_L \end{aligned}$$

$$\begin{aligned} I_{RMS} &= \frac{I_m}{2} \\ I_m &= \frac{V_m}{R_L} \end{aligned}$$

5) DC output power (P_{dc}) :-

$$\begin{aligned}P_{dc} &= I_{dc}^2 R_L \\&= \left(\frac{I_m}{\pi}\right)^2 R_L = \frac{I_m^2}{\pi^2} R_L \\&= \left(\frac{V_m}{R_L}\right)^2 \cdot \frac{1}{\pi^2} R_L \\&= \frac{V_m^2}{R_L^2 \pi^2} \cdot \cancel{R_L}\end{aligned}$$

$$\boxed{P_{dc} = \left(\frac{V_m}{\pi}\right)^2 \cdot \frac{1}{R_L}}$$

6) AC output power (P_{ac}) :-

$$P_{ac} = I_{RMS}^2 R_L$$

$$P_{ac} = \left(\frac{I_m}{2} \right)^2 R_L$$

8) Ripple factor (γ):-

Ripple factor is defined as the ratio of RMS value of the ac component present in the rectified output to the dc component present in the rectified output.

$$\gamma = \frac{\text{RMS value of ac Component of o/p}}{\text{dc Component of o/p}}$$

$$\begin{aligned}
 &= \sqrt{\frac{I_{RMS}^2}{I_{dc}^2} - 1} &= \sqrt{\frac{(\cancel{I_m}/2)^2}{(\cancel{I_m}/\pi)^2} - 1} \\
 &= \sqrt{\frac{\frac{1}{4}}{\frac{1}{\pi^2}} - 1} &= \sqrt{\frac{\pi^2}{4} - 1}
 \end{aligned}$$

$$\gamma = 1.21$$

This indicates that the **amount of ac present in the output is 121 % of the dc voltage.**

7) Rectification efficiency (η):-

The rectifier efficiency is defined as the ratio of output dc power to input ac power.

$$\eta = \frac{\text{DC o/p power}}{\text{AC I/p power}} = \frac{P_{dc}}{P_{ac}} = \frac{\frac{I_m^2}{\pi^2} R_L}{\frac{I_m^2}{4} R_L} = \frac{\frac{1}{\pi^2}}{\frac{1}{4}} = \frac{1}{\pi^2} \times \frac{4}{1}$$

$$\eta = 0.406$$

$$\boxed{\% \eta = 40.6\%}$$

In HWR, maximum 40.6% ac power gets converted to dc power in the load.

Advantages of HWR :-

1. Only one diode is required.
 2. No centre-tap is required on the transformer.
 3. PIV is same as secondary output voltage.
-

Disadvantages or demerits of HWR :-

1. The ripple factor is too high i.e. ≈ 1.21
 2. Rectification efficiency is low i.e. 40.6%.
-

FWR with centre-tapped transformer :-

❖ Explain with the help of a circuit diagram the working of a full wave rectifier

Derive expressions for


i) I_{dc}

ii) I_{rms}

iii) V_{dc}

iv) Ripple factor

v) Rectifier efficiency.

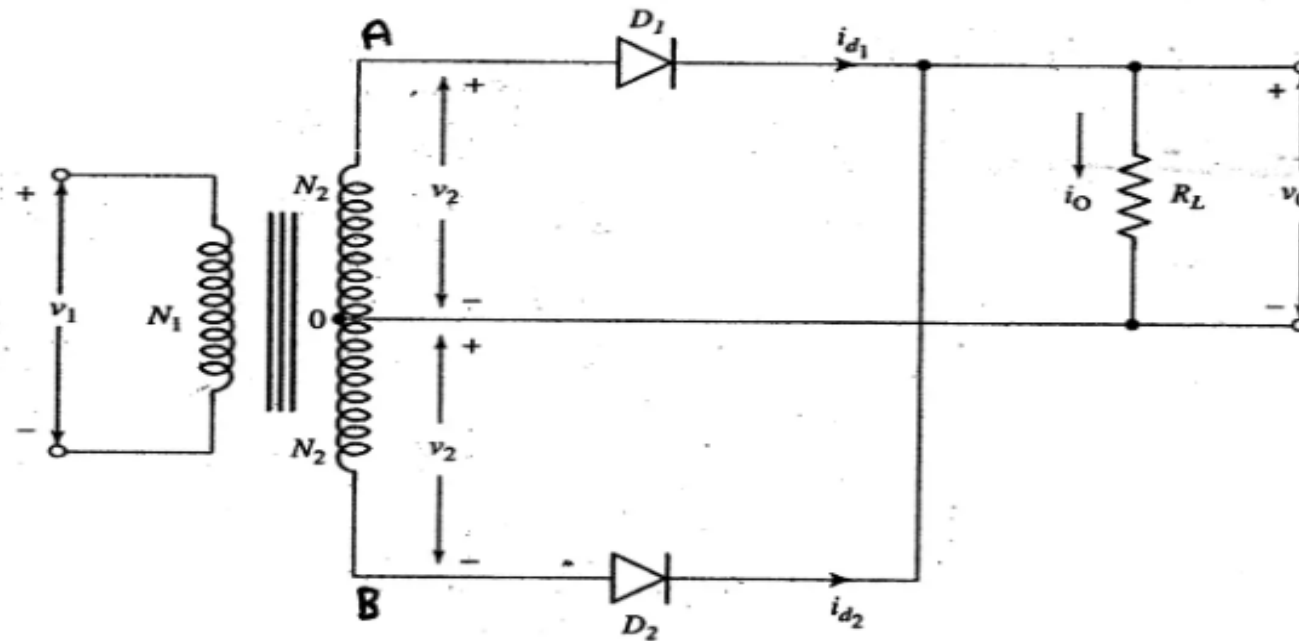

Jan-10,5M

Figure 1. FWR using two diodes & a centre-tapped transformer.

Operation :-

During +ve half cycle :-

❖ During +ve half cycle of the ac input voltage, end A becomes +ve with respect to end B. the diode ' D_1 ' is forward biased and conducts while the diode D_2 is reverse biased and acts as open circuit and will not conduct as shown in fig 2.

❖ The diode **D_1** supplies the load current. The conventional **current flow** is through diode **D_1** , load resistor **R_L** & the **upper half of secondary winding** as shown by the **dotted arrows**.

During -ve half cycle :-

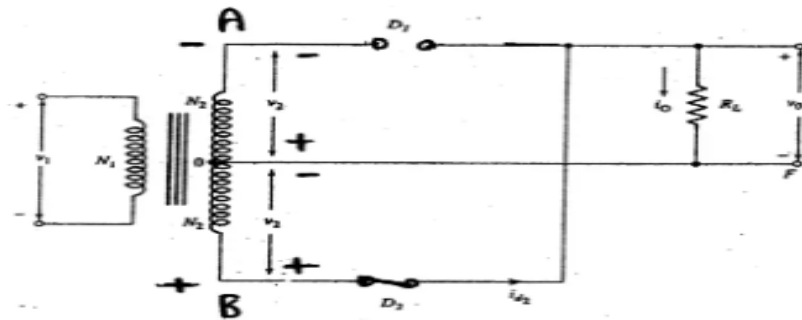


Fig 3.


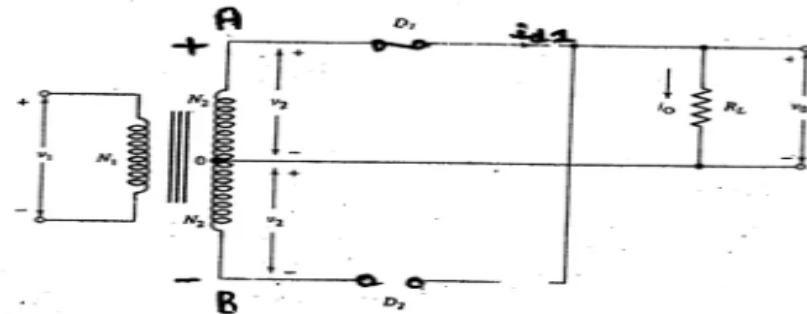


Fig 2.

- ❖ During -ve half cycle of the ac input voltage, end A becomes -ve with respect to end B, the diode ' D_2 ' is forward biased and conducts while the diode D_1 is reverse biased and acts as open circuit and will not conduct as shown in fig 3.
- ❖ The diode **D_2 supplies the load current**. The conventional **current flow** is through diode **D_2** , load resistor **R_L** & the **lower half of secondary winding** as shown by the **solid arrows**.
- ❖ From fig 2 & 3 it can be observed that **current** in the **load R_L** is in the **same direction** for **both half cycles** of **ac input voltage**.
 - ❖ For both the half cycles the current flows through load in the same direction. Hence we get two half cycles for one complete input signal.

I/O Waveforms

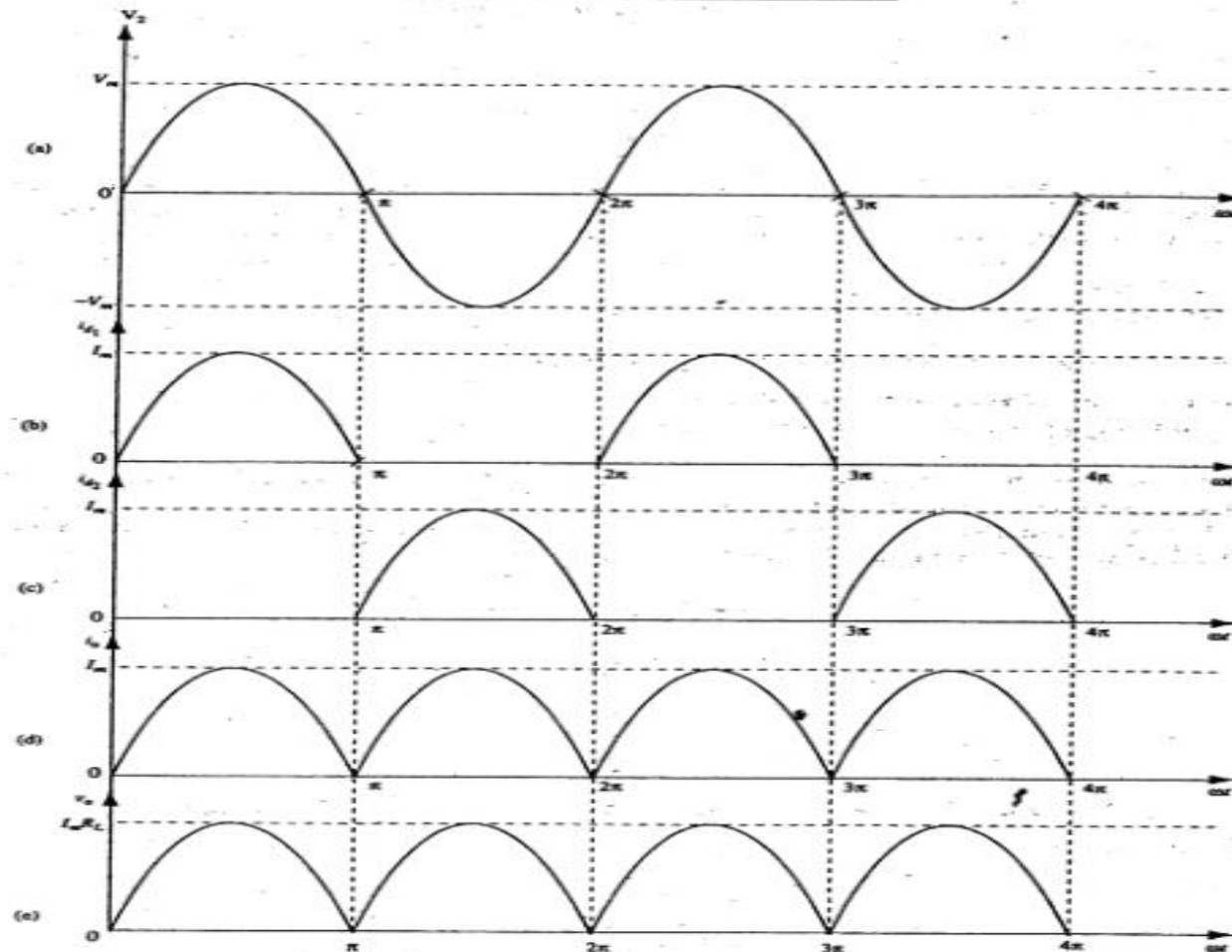

Voltage and current waveforms. (a) Secondary voltage waveform, (b) & (c) Diode current waveforms, (d) load current waveform, (e) load voltage waveform.

1) **Average or dc load current (I_{dc} or I_{av}) :-**

Consider one cycle of the load current I_L from 0 to π to obtain the average value which is dc value of load current.

$$\begin{aligned} I_{dc} &= \frac{1}{\pi} \int_0^{\pi} I_L d\omega t \\ &= \frac{1}{\pi} \int_0^{\pi} I_m \sin \omega t d\omega t \\ &= \frac{I_m}{\pi} \left[-\cos \omega t \right]_0^{\pi} \\ &= \frac{I_m}{\pi} \left[-\cos(\pi) - \{-\cos(0)\} \right] \end{aligned}$$

$$= \frac{I_m}{\pi} [1+1]$$

$$I_{dc} = \frac{2I_m}{\pi}$$

2) Average dc load voltage (V_{dc}) :-

$$\begin{aligned} V_{dc} &= I_{dc} R_L \\ &= \frac{2I_m}{\pi} R_L \\ &= \frac{2V_m}{\pi \cancel{R_L}} \cdot \cancel{R_L} \end{aligned}$$

$$V_{dc} = \frac{2V_m}{\pi}$$

$I_{dc} = \frac{2I_m}{\pi}$
$I_m = \frac{V_m}{R_L}$

3) RMS value of load current (I_{RMS}) :-

$$I_{RMS} = \sqrt{\frac{1}{\pi} \int_0^{\pi} I_L^2 d\omega t} = \sqrt{\frac{1}{\pi} \int_0^{\pi} I_m^2 \sin^2 \omega t d\omega t}$$

$$= I_m \sqrt{\frac{1}{\pi} \int_0^{\pi} \left(\frac{1 - \cos 2\omega t}{2} \right) d\omega t}$$

$$\therefore \sin^2 \theta = \frac{1 - \cos 2\theta}{2}$$

$$= I_m \sqrt{\frac{1}{2\pi} \left\{ \int_0^{\pi} 1 d\omega t - \int_0^{\pi} \cos 2\omega t d\omega t \right\}}$$

$$= I_m \sqrt{\frac{1}{2\pi} \left\{ [\omega t]_0^{\pi} - \left[\frac{\sin 2\omega t}{2} \right]_0^{\pi} \right\}}$$

$$\therefore \int \cos 2\theta d\theta = \frac{\sin 2\theta}{2}$$

$$= I_m \sqrt{\frac{1}{2\pi} \left\{ [\pi - 0] - \frac{1}{2} [\sin 2(\pi) - \sin 2(0)] \right\}}$$

$$= I_m \sqrt{\frac{1}{2\pi} \left\{ \pi - \frac{1}{2} [0 - 0] \right\}}$$

$$\boxed{I_{RMS} = \frac{I_m}{\sqrt{2}}}$$

4) RMS value of the load voltage (V_{RMS}) :-

$$V_{RMS} = I_{RMS} R_L$$

$$V_{RMS} = \frac{I_m}{\sqrt{2}} R_L$$

5) DC output power (P_{dc}) :-

$$P_{dc} = I_{dc}^2 R_L$$

$$= \left(\frac{2I_m}{\pi} \right)^2 R_L$$

$$P_{dc} = \frac{4}{\pi^2} I_m^2 R_L$$

$$I_{dc} = \frac{2I_m}{\pi}$$
$$I_m = \frac{V_m}{R_L}$$

6) AC output power (P_{ac}) :-

$$P_{ac} = I_{RMS}^2 R_L$$
$$= \left(\frac{I_m}{\sqrt{2}} \right)^2 R_L$$

$$P_{ac} = \frac{I_m^2}{2} R_L$$

$$I_{RMS} = \frac{I_m}{\sqrt{2}}$$

The rectifier efficiency is defined as the ratio of output dc power to input ac power.

7) Rectification efficiency (η) :- \rightarrow

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{\frac{4}{\pi^2} I_m^2 R_L}{\frac{I_m^2}{2} R_L} = \frac{\frac{4}{\pi^2}}{\frac{1}{2}} = \frac{4}{\pi^2} \times \frac{2}{1} = 0.812$$

$$\% \eta = 81.2\%$$

8) Ripple factor (γ):-

$$\gamma = \sqrt{\frac{I_{RMS}^2}{I_{dc}^2} - 1}$$

$$\gamma = \sqrt{\left[\frac{\left(\frac{I_m}{\sqrt{2}}\right)^2}{\left(\frac{2I_m}{\pi}\right)^2} \right] - 1}$$

$$= \sqrt{\left[\frac{\frac{\cancel{I_m^2}}{\cancel{2}}}{\frac{4\cancel{I_m^2}}{\pi^2}} \right] - 1} = \sqrt{\left(\frac{\frac{1}{2}}{\frac{4}{\pi^2}} \right) - 1}$$

$$= \sqrt{\left(\frac{1}{2} \times \frac{\pi^2}{4} \right) - 1}$$

$$= \sqrt{\frac{\pi^2}{8} - 1}$$

$$\boxed{\gamma = 0.48}$$

This indicates that the amount of ac present in the output is **0.48 %** of the dc voltage.


Advantages of FWR :-

1. The efficiency is twice that of HWR i.e. 81.2%
 2. The ripple factor is much less than that of HWR
 3. The dc output voltage and load current value are twice than HWR.
 4. Large dc power output.
-
-

Disadvantages of FWR :-

1. PIV of diode the is higher.
2. Cost of centre-tap transformer is higher.
3. Output voltage is half of the secondary voltage.


FULL WAVE BRIDGE Rectifier (FWBR) :-

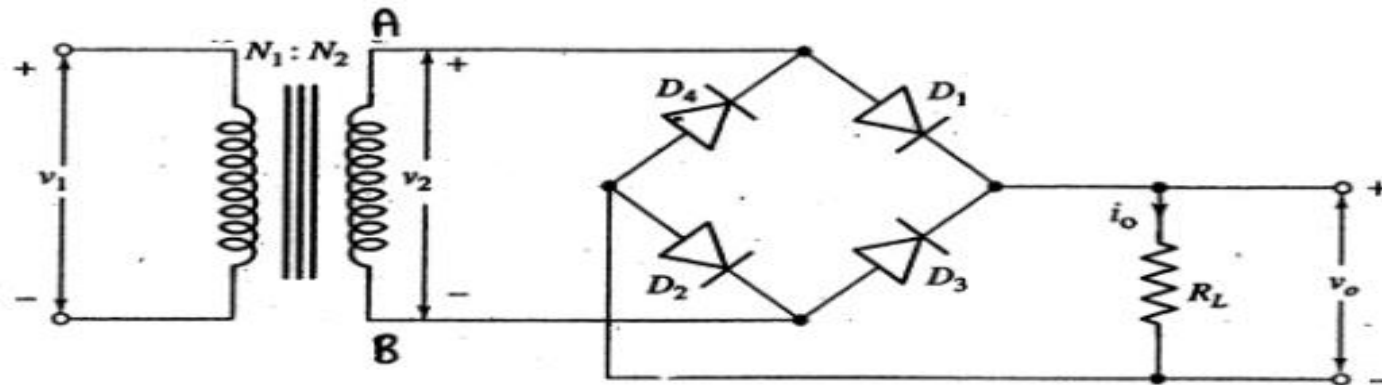

Full-wave bridge rectifier.

Operation :-


During +ve half cycle :-

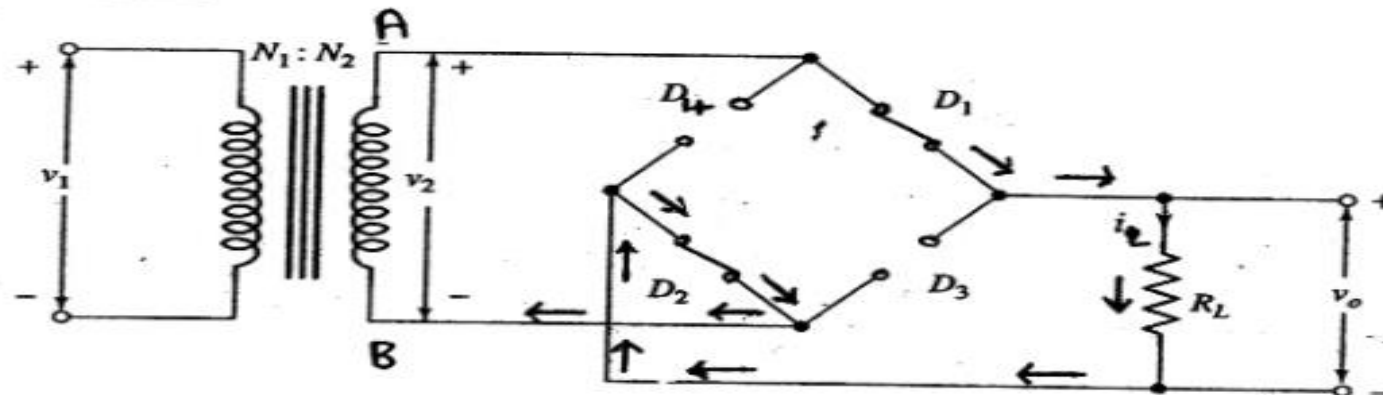

- ❖ During **+ve half cycle** of the ac input voltage, end A becomes +ve with respect to end B. This makes diodes **D_1 & D_2 forward biased**, while **D_3 & D_4 are reverse biased**.

Therefore only **diodes D_1 & D_2 conducts**. The conventional **current flows** through the **load resistance R_L** and is shown by the **arrows**.


During -ve half cycle :-

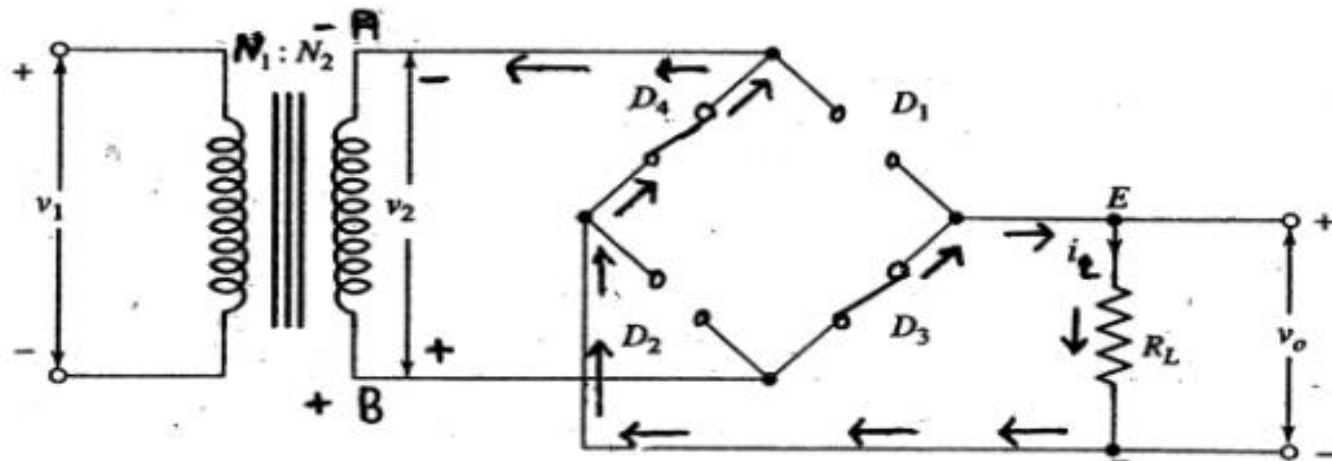

- ❖ During -ve half cycle of the ac input voltage, end A becomes -ve with respect to end B. This makes diodes **D_3 & D_4 forward biased**, while **D_1 & D_2 are reverse biased**.

Therefore only **diodes D_3 & D_4 conducts**. The conventional **current flows** through the **load resistance R_L** and is shown by the **arrows**.

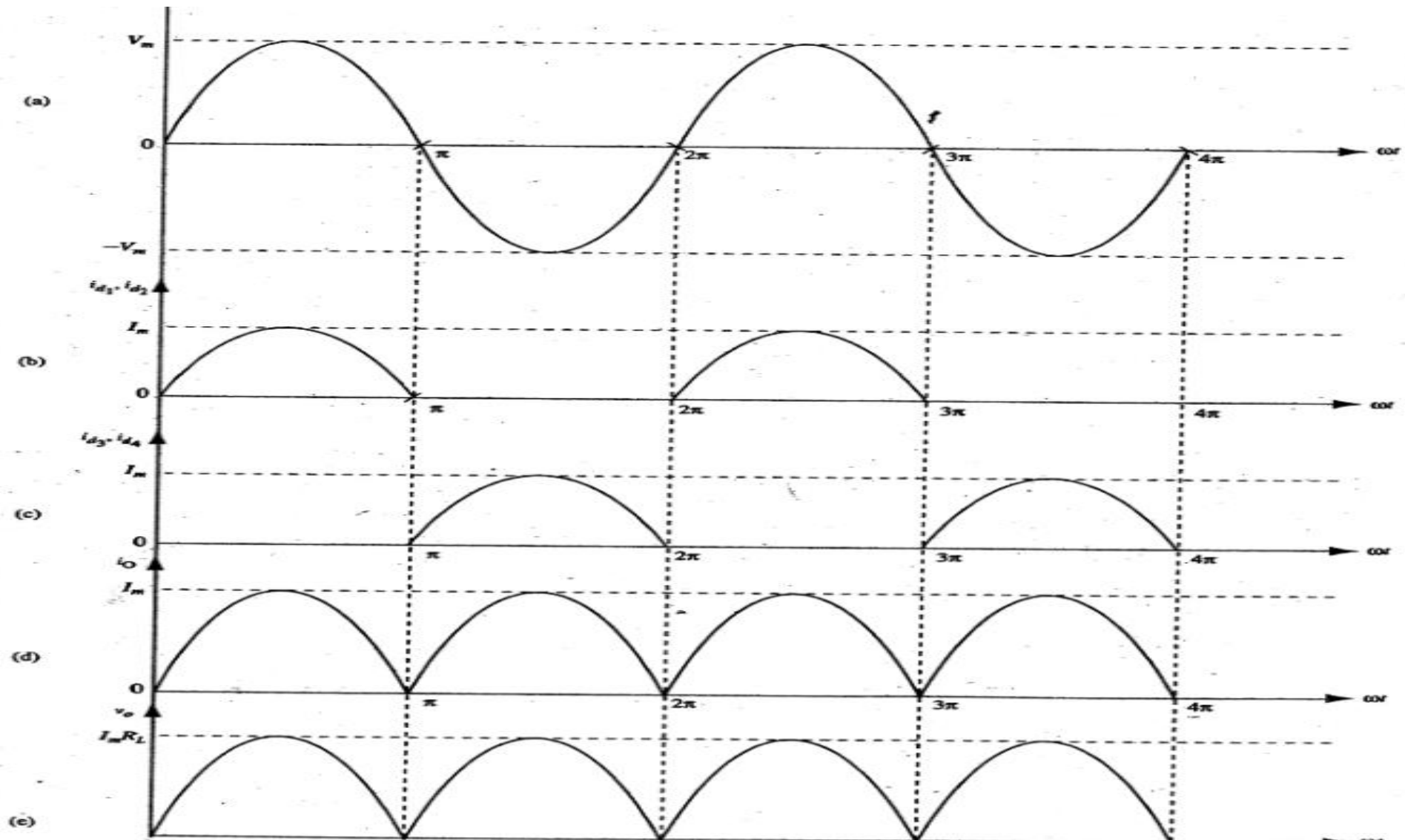- ❖ For both the half cycles the current flows through load in the same direction. Hence we get two half cycles for one complete input signal.



- ❖ In a full wave bridge rectifier, the transformer secondary voltage is $100\sin\omega t$. The forward resistance of each diode is 25Ω and the load resistance is 950Ω . Calculate
- i) D.C. output voltage ii) ripple factor iii) Efficiency of rectification
- iv) PIV across non-conducting diodes.

Jan-2003, 8M

Given: $V_s = 100 \sin\omega t$, $R_f = 25\Omega$, $R_L = 950\Omega$

WKT $V_s = V_m \sin\omega t$ $V_m = 100V$

Sol:-

$$* I_m = \frac{V_m}{2R_f + R_L} = \frac{100}{(2 \times 25) + 950} = 0.1A$$

$$* I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 0.1}{\pi} = 0.063A$$

$$i) V_{dc} = I_{dc} R_L = 0.063 \times 950 = 59.85V$$

$$\text{ii)} \quad \gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{\left(\frac{0.0707}{0.063}\right)^2 - 1} = 0.048$$

$$I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{0.1}{\sqrt{2}} = \underline{0.0707A}$$

$$\text{iii)} \quad P_{dc} = I_{dc}^2 R_L = (0.063)^2 \times 950 = 3.85W$$

$$\begin{aligned} P_{ac} &= (I_{rms})^2 \times (2R_f + R_L) \\ &= (0.070)^2 [(2 \times 25) + 950] \end{aligned}$$

$$P_{ac} = 5W$$

$$\text{iv)} \quad \% \eta = \frac{P_{dc}}{P_{ac}} \times 100 = \frac{3.85W}{5W} \times 100 = 77\%$$

- ❖ In a two diode FWR circuit, the voltage across each half of the transformer secondary is 100V. The load resistance is 950Ω and each diode has a forward resistance of 50Ω . Find the load current and the rms value of the input current.

June-2004, 6M

Given: $V_s = 100V$, $R_f = 50\Omega$, $R_L = 950\Omega$.

$$* V_m = \sqrt{2} \times 100 = 141.42V$$

$$* I_m = \frac{V_m}{R_f + R_L} = \frac{141.42V}{950\Omega + 50\Omega} = 0.141A$$

$$* I_{RMS} = \frac{I_m}{\sqrt{2}} = \frac{0.141}{\sqrt{2}} = 0.0997A$$

$$* I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 0.141}{\pi} = 0.090A$$

❖ A bridge rectifier is driving a load resistance of 100Ω . It is driven by a source voltage of 230V , 50Hz . Neglecting diode resistances. Calculate.

i) Average DC voltage
output waveform.

ii) Average direct current

iii) frequency of

Jan-2005, 6M

Given : $R_L = 100\Omega$, $V_s = 230\text{V}$, $f = 50\text{Hz}$

Sol:- $V_m = \sqrt{2} \times V_s = \sqrt{2} \times 230 = \underline{325\text{V}}$

i) $V_{dc} = \frac{2V_m}{\pi} = \frac{2 \times 325}{\pi} = \underline{206.9\text{V}}$

ii) $I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 3.25}{\pi} = \underline{2.06\text{A}}$

iii) O/p Frequency = $2f_{in} = 2 \times 50\text{Hz} = \underline{100\text{Hz}}$

Where $I_m = \frac{V_m}{R_L} = \frac{325\text{V}}{100\Omega}$

$I_m = 3.25\text{A}$

- ❖ In a full wave rectifier, the input is from a 30-0-30v transformer. The load and diode forward resistance are 100Ω and 10Ω respectively. Calculate the average voltage, rectification efficiency and percentage regulation.

June-07, 7M

Given : $V_S = 30\text{V}$, $R_L = 100\Omega$, $R_f = 10\Omega$.

$$* V_m = \sqrt{2} V_S = \sqrt{2} \times 30 = \underline{42.4264\text{V}}$$

$$* I_m = \frac{V_m}{R_f + R_L} = \frac{42.4264\text{V}}{(100 + 10)\Omega} = \underline{0.3856\text{A}}$$

$$* I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 0.3856}{\pi} = \underline{0.2455\text{A}}$$

$$* V_{dc} = I_{dc} R_L = 0.2455 \times 100 = \underline{24.55\text{V}}$$

$$* P_{dc} = I_{dc}^2 R_L = (0.2455)^2 \times 100 = \underline{6.027\text{W}}$$

$$* P_{ac} = I_{rms}^2 (R_f + R_L) = (0.272)^2 (10 + 100) \Omega = \underline{8.177 W}$$

$$* I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{0.3856}{\sqrt{2}} = \underline{0.272 A}$$

$$* \% \eta = \frac{P_{ac}}{P_{ac}} \times 100 = \frac{6.027 W}{8.177 W} = \underline{73.69 \%}$$

$$* \% \text{ Regulation} = \frac{R_f}{R_L} \times 100 = \frac{10}{100} \times 100 = \underline{10}$$

Rectifiers with C-filters

❖ What is a filter ? Why it is required.


Filter is a **circuit** used to **reduce** the **ripple** content **present in** the **rectified output**. The ripple content of rectified output can be filtered out by connecting a capacitor in parallel with R_L .

The **output from rectifiers** is **not pure dc due** to **ripple** content. In **HWR** ripple content is **121%**, whereas in **FWR** it is **48%**. In order to obtain **pure dc** **filter circuits are required**


Filter is a **circuit** used to **reduce** the **ripple** content **present in** the **rectified output**. The ripple content of rectified output can be filtered out by connecting a capacitor in parallel with R_L .

The **output from rectifiers** is **not pure dc** due to **ripple** content. In **HWR** ripple content is **121%**, whereas in **FWR** it is **48%**. In order to obtain **pure dc**, **filter circuits** are **required**.

HWR with capacitor filter :-

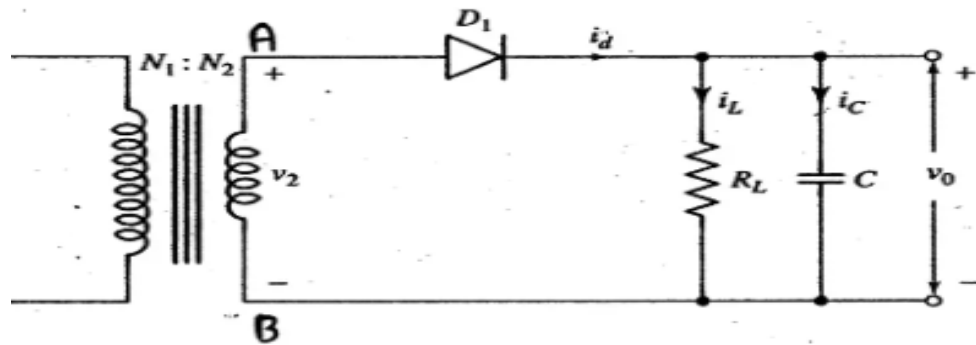

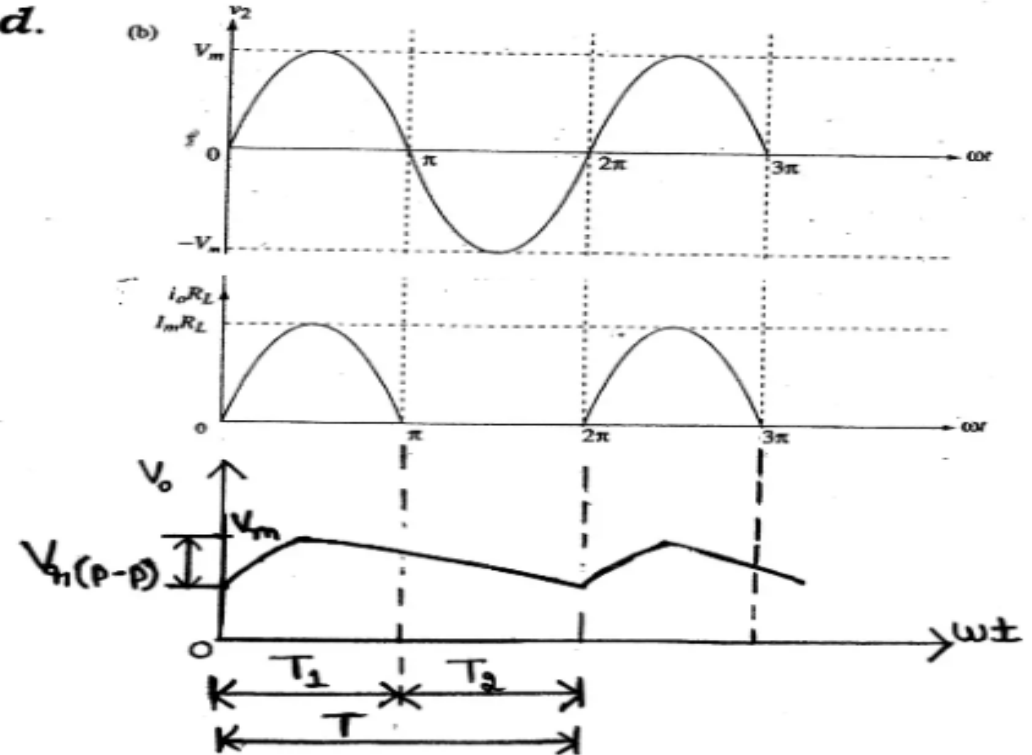Half-wave rectifier with capacitor filter.



During +ve half cycle of the ac input, the diode is forward biased and conducts and charges the capacitor to the peak value of V_m of the input voltage. When the input voltage falls below V_m , the diode stops conducting.

Now, the **capacitor starts discharging** through R_L and the **capacitor voltage decreases**. The **discharging** of capacitor **continues** till the **diode starts conducting again** and **charges** the **capacitor** in the **next +ve half cycle** of the ac **input** voltage.

From figure 2, we find that **without capacitor filter**, output voltage varies between **zero** and V_m . **With capacitor filter**, the **output voltage** varies between $(V_m - V_{r(p-p)})$ and V_m .

This clearly indicates that the **shunting** of R_L by '**C**' **reduces** the **ripple** content in the output voltage. The ripple factor with '**C**' filter is given by

$$\gamma = \frac{1}{2\sqrt{3} f_c R_L}$$

