



## School of Engineering and Technology

**Subject: BEEE**

**Subject Code: 24BEELY104**

### UNIT 3

#### Sample Questions:


**2 Marks**

- ✓ Mention any two applications of PN diode?
- ✓ Why a series resistor is necessary when a diode is forward biased?
- ✓ What is hole and electron in p-n junction diode?
- ✓ What are the two types of semiconductors?
- ✓ What are the main types (any two) of diodes?
- ✓ What are the three regions in which diodes function?
- ✓ What is a PN Junction? How is it formed?
- ✓ What are the types of extrinsic semiconductor?
- ✓ Define extrinsic semiconductor.
- ✓ Define intrinsic semiconductor.
- ✓ What is P-type semiconductor?
- ✓ What is N-type semiconductor?
- ✓ Define doping.
- ✓ Define biasing and mention the types of biasing?
- ✓ What is meant by forward bias?
- ✓ What is meant by reverse bias?
- ✓ What is depletion region?
- ✓ Mention one application of zener diode?
- ✓ For a Half wave rectifier the minimum number of diodes required is \_\_\_\_\_
- ✓ For a centre tapped full wave rectifier the minimum number of diodes required is \_\_\_\_\_
- ✓ The maximum efficiency of a half wave rectification is \_\_\_\_\_
- ✓ The maximum efficiency of a full wave rectification is \_\_\_\_\_
- ✓ Define efficiency of a rectifier.
- ✓ Photodiode is used to detect \_\_\_\_\_ light.


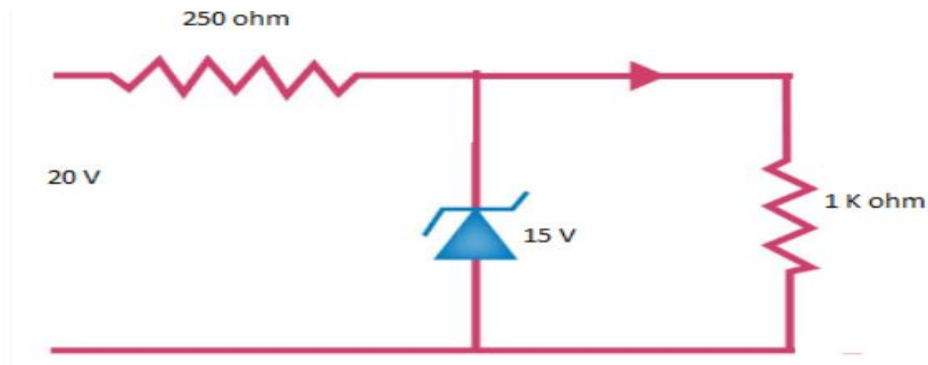
## School of Engineering and Technology

- ✓ A Zener diode, having breakdown voltage equal to 15 V, is used in a voltage regulator circuit shown in the figure. The current through the diode is



### Sample Questions:

**5 Marks**

- ✓ Explain PN junction diode with necessary equations and diagrams?
- ✓ Draw the equivalent circuit of PN junction diode?
- ✓ Draw the VI characteristics of a PN junction diode.
- ✓ Write short notes on: (i) Photodiode (ii) Photo coupler
- ✓ Differentiate between half wave and full wave rectifiers (consider 5 parameters).
- ✓ Show that the average or DC load current ( $I_{dc}$  or  $I_{av}$ ) of a half wave rectifier is  $I_m/\pi$ .
- ✓ Show that the average or DC load current ( $I_{dc}$  or  $I_{av}$ ) of a half wave rectifier is  $2I_m/\pi$ .
- ✓ Compare zener breakdown and avalanche breakdown (consider 5 parameters).
- ✓ Show that the root mean square value of the load current  $I_{rms} = 0.707 I_m$ .
- ✓ A half-wave rectifier is used to supply 50V d.c. to a resistive load of 800  $\Omega$ . The diode has a resistance of 25  $\Omega$ . Calculate a.c. voltage required.

### Sample Questions:


**10Marks**

- ✓ What is a PN junction diode? With a neat diagram explain the forward and reverse characteristics of PN junction diode?


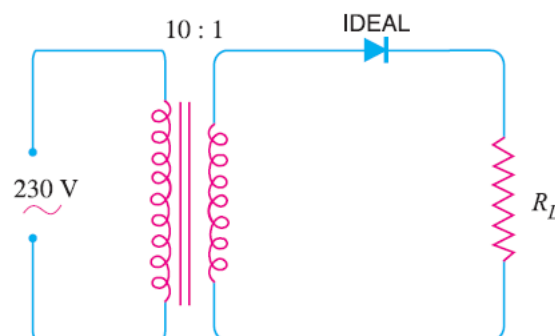
## School of Engineering and Technology


- ✓ With necessary waveforms and circuit diagram explain the working of a half wave rectifier?
- ✓ With necessary waveforms and circuit diagram explain the working of a full wave rectifier with capacitive filter?
- ✓ With an appropriate circuit explain how zener diode can be used as voltage regulator?
- ✓ A diode used as a half wave rectifier whose internal resistance is  $20\Omega$  is to supply power to  $1000\Omega$  load from  $110V_{rms}$  source of supply. Calculate Peak load current, DC load current, AC load current, DC power, AC input power, Rectification efficiency.
- ✓ In a center tapped FWR, the rms half wave secondary voltage is  $10V$ . Assuming ideal Diode and load resistance of  $R_L = 2K\Omega$  Find peak current, DC load voltage, ripple factor, efficiency of rectification.
- ✓ A half wave rectifier is connected to a transformer with turns ratio  $4:1$  find its average DC output voltage, PIV of diode and ripple frequency if input voltage is  $200 V$  rms,  $50$  Hz mains supply.
- ✓ An a.c. supply of  $230 V$  is applied to a half-wave rectifier circuit through a transformer of turn ratio  $10: 1$ . Find (i) the output d.c. voltage and (ii) the peak inverse voltage. Assume the diode to be ideal.




- ✓ An a.c. voltage of peak value  $20 V$  is connected in series with a silicon diode and load resistance of  $500\Omega$ . If the forward resistance of diode is  $10 \Omega$ , find : (i) peak current through diode (ii) peak output voltage. What will be these values if the diode is assumed to be ideal?



## School of Engineering and Technology

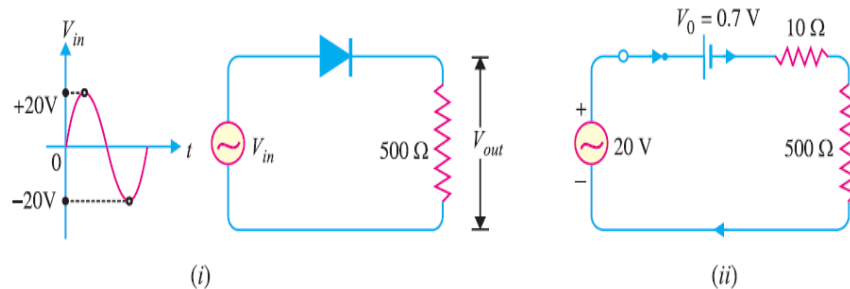

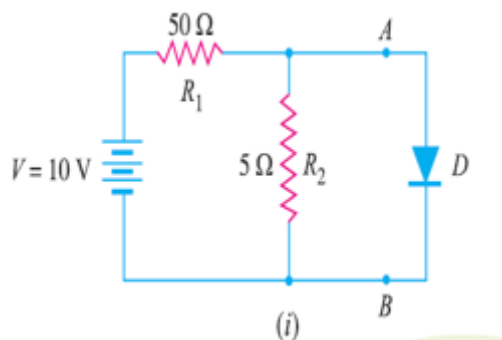Find the current through the diode in the circuit shown in Fig. (i). Assume the diode to be ideal.



A crystal diode having internal resistance  $r_f = 20\Omega$  is used for half-wave rectification.

If the applied voltage  $v = 50 \sin \omega t$  and load resistance  $R_L = 800\Omega$ , find:

- (i)  $I_m$ ,  $I_{dc}$ ,  $I_{rms}$
- (ii) a.c. power input and d.c. power output
- (iii) d.c. output voltage
- (iv) Efficiency of rectification.

**Note: In Rectifiers topic study only half wave, full wave and half wave rectifier with capacitive filter.**